
 
 



Practice Problems for Chapter 5 and 6

 - 1) Write the output expression for the logic circuit in the figure below. Implement the logic
- using only NAND gates
 - using only NOR gates.




- 2) Given the following truth table, find out the binary expression for output F in standard SOP form. Simplify the expression and reduce it to SOP form using Karnaugh Map. Create the NAND/NAND two-level implementation for the minimized SOP expression.

A	B	C	D	F
0	0	0	0	0
0	0	0	1	0

 

$$\bar{A}\bar{B}\bar{C}\bar{D} + A\bar{C}D + \bar{B}C + A\bar{B}$$


0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

 

 - 3) Explain what is the difference between a half adder's function, inputs and outputs and a full-adder's. Consider you want to design a circuit to add two 4-bit numbers, and you have half adders and full adders available to use as components.
- Draw a block diagram of your 4-bit adder, using half and full adders. Do not draw a gate-level diagram. Show and label all inputs and outputs.
 - Assume that a half adder has a maximum propagation delay of δ , and a full adder has a maximum propagation delay of 2δ . What is the maximum propagation delay for your 4-bit adder, from LSB input to MSB output?

Half adder only has 2-1 Bit inputs and outputs a sum with a carry.


A full adder is much the same except they have a carry input.



max delay

$$6\Delta + 1\Delta = 7\Delta$$

 
- 4) The data input and data select waveforms as shown below are applied to the multiplexer as shown in figure below. Determine the output waveform Y in relation to the inputs.



- 5) Implement the Boolean function represented by following truth table with a 1 of 8 multiplexer.


A	B	C	D	F
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0

$f = D$

 


0	0	1	1	1	$F=D$
0	1	0	0	1	$F=\bar{D}$
0	1	0	1	0	$F=0$
0	1	1	0	0	$F=0$
0	1	1	1	0	$F=D$
1	0	0	0	0	$F=0$
1	0	0	1	0	$F=D$
1	0	1	0	0	$F=1$
1	0	1	1	1	$F=1$
1	1	0	0	1	
1	1	0	1	1	
1	1	1	0	1	
1	1	1	1	1	

 - 6) For the parallel adder in figure below, determine the sum by analysis of the logical operation of the circuit.



 - 7) For the multiplexer in figure below, are sequenced by the waveform as below. If $D_0 = 1$, $D_1 = 0$, $D_2 = 0$, and $D_3 = 1$, determine the output waveform.



100110010011