

Problem No. 1: (25 points)

What is the difference between a POS expression and an SOP expression?

SOP

A Boolean expression consisting of a set of min-terms. The expression is built with each product term that gives a high, or 1, output. The final expression is obtained by adding the relevant product terms.

POS

A Boolean expression consisting of a set of max-terms. The expression is built with each input combination that results in a low, or 0, output. The final expression is obtained by multiplying the relevant sum terms.

For the truth table given below, derive a standard SOP and a standard POS expression. No simplification required.

SOP

$$ABC\bar{D} + A\bar{B}C\bar{D} + \bar{A}\bar{B}C\bar{D} + \bar{A}\bar{B}C\bar{D} + \bar{A}\bar{B}C\bar{D} + \bar{A}\bar{B}C\bar{D} + \bar{A}\bar{B}C\bar{D}$$


POS

$$\begin{aligned} & \cancel{(A+B+C+D)} \cancel{(A+B+C+D)} \cancel{(A+B+C+D)} \cancel{(A+B+C+D)} \\ & \cancel{(A+B+C+D)} \cancel{(A+B+C+D)} \cancel{(A+B+C+D)} \cancel{(A+B+C+D)} \\ & (A+B+C+D)(A+B+C+D)(A+B+C+D)(A+B+C+D) \\ & (\bar{A}+B+C+D)(\bar{A}+B+C+D)(\bar{A}+B+C+D)(\bar{A}+B+C+D) \end{aligned}$$


A	B	C	D	F
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

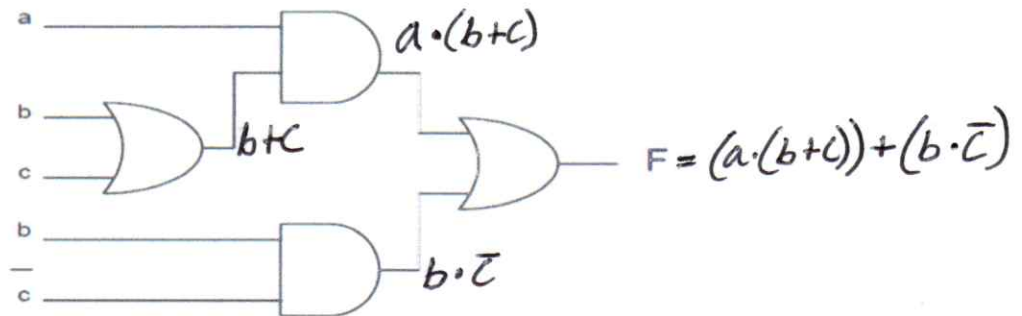Problem No. 2: (25 points)

Find the Boolean expression for the output of the circuit F . Do not simplify.




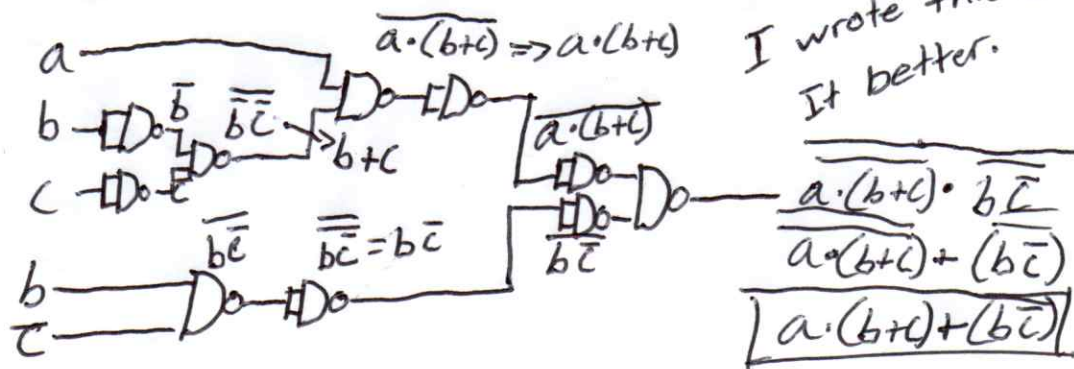
Why are NAND gates and NOR gates called *Universal Gates*? For the circuit given above, implement the logic using *only NAND gates*.



NAND and NOR gates are called the universal gates because they can perform all the basic functions AND, OR, NOT. All logic circuits can be converted into NAND/NOR logic.

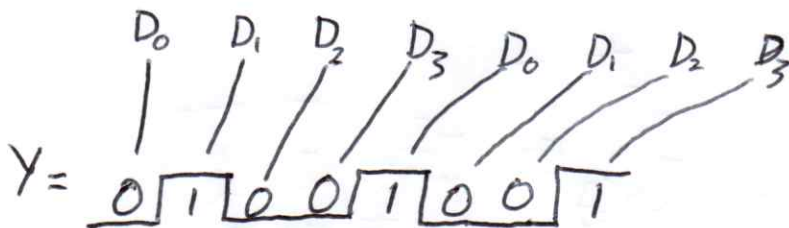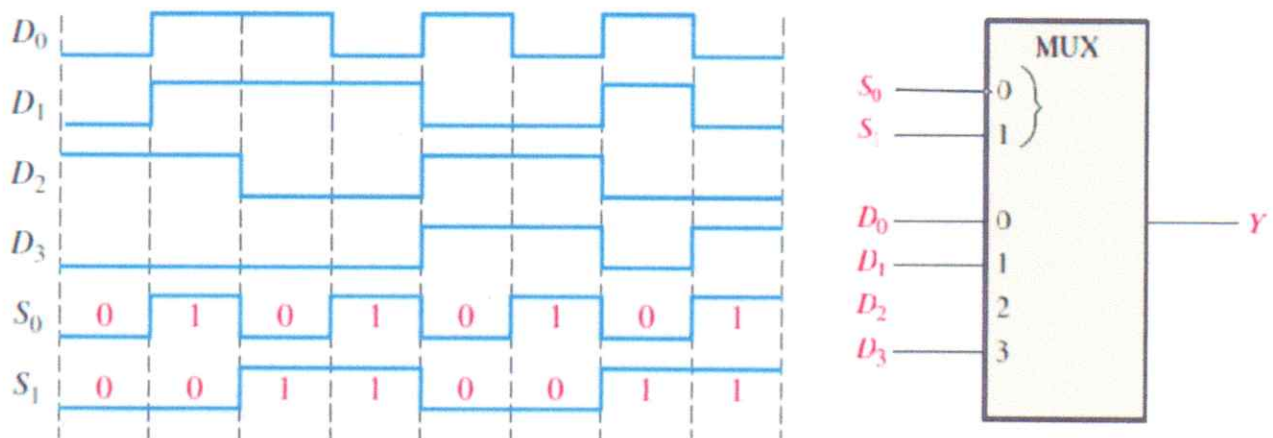
Problem No. 3: (25 points)

The data input and data select waveforms as shown below are applied to the 1 of 4 multiplexer as shown in figure below. Determine the *output waveform Y* in relation to the inputs.



Consider the logic function described by the following truth table. *Implement* the logic function specified in the truth table by using a *1-of-4 MUX*. Make sure to clearly label all inputs and outputs.


	X	Y	Z	F	
0	0	0	0	0	$F=Z$
	0	0	1	1	
1	0	1	0	1	$F=\bar{Z}$
	0	1	1	0	
2	1	0	0	0	$F=0$
	1	0	1	0	
3	1	1	0	1	$F=1$
	1	1	1	1	

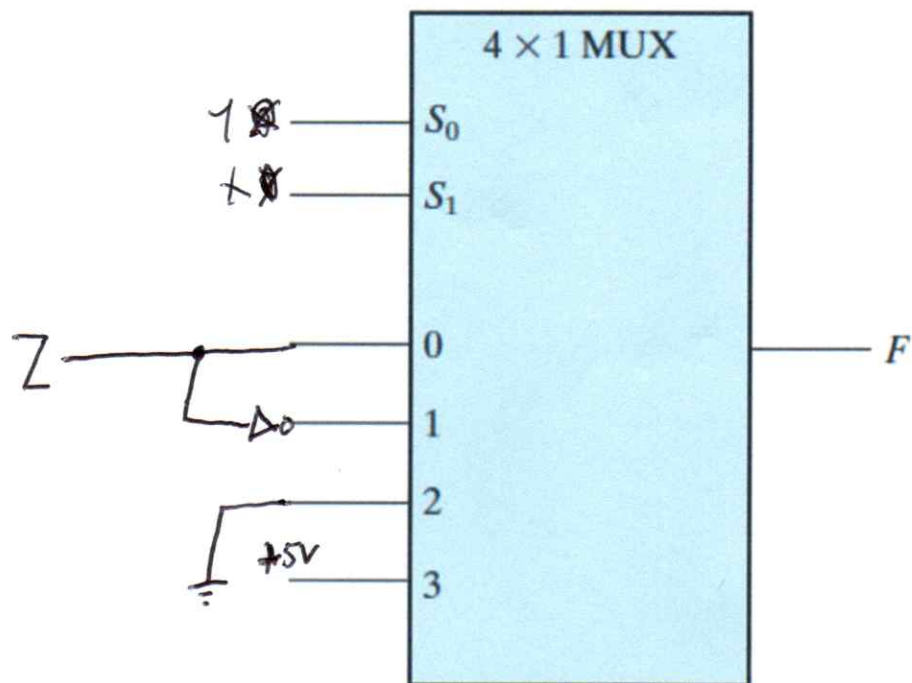


Problem No. 4: (25 points)

Figure below shows a schematic of a full-adder and the corresponding truth table.

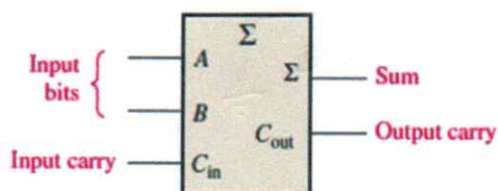Based on the truth table, write the SOP expressions for the Σ and C_{out} of the full-adder.




A	B	C_{in}	C_{out}	Σ
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

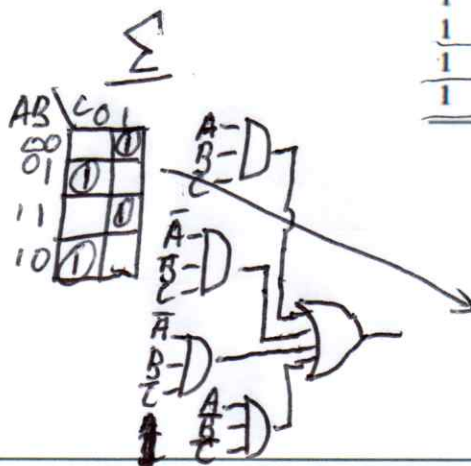

$$C_{out} = \bar{A}\bar{B}C_{in} + A\bar{B}C_{in} + AB\bar{C}_{in} + ABC_{in}$$

$$\Sigma = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC$$

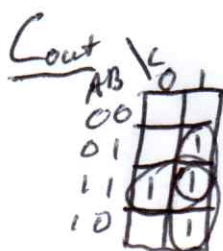Use a Karnaugh map to minimize the expressions and show how to implement the circuits for the Σ and C_{out} using inverters and AND-OR logic.



$$C_{out} = BC + AC + AB$$

